SENSORS & AUTOMATION


Experiment No:- 6: Ladder Diagram for On/OFF application.

APPLICATIONS:

- 1) It can be used in decorative lights used in Diwali.
- 2) Nowadays even the lights used in homes have functionalities to change light from yellow to white which can be done using this.
- 3) Any place where random lighting is required can be achieved using this.


❖ ON/OFF SWITCH (2 PUSH BUTTONS)

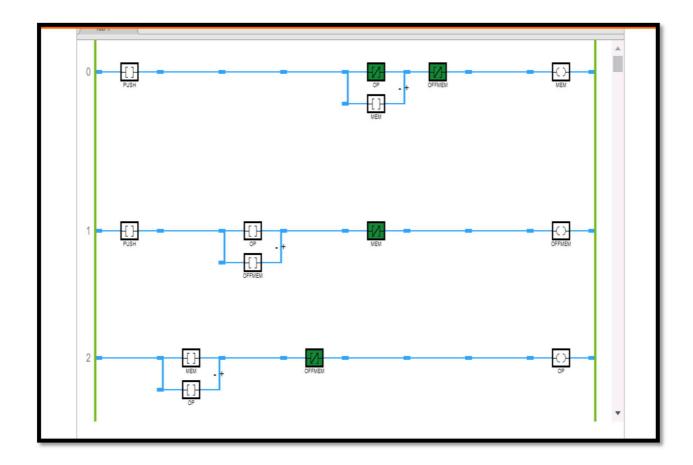1) When both are not toggled all outputs are OFF.




2) When both are toggled, we get 2 conditions.


a) One light is ON

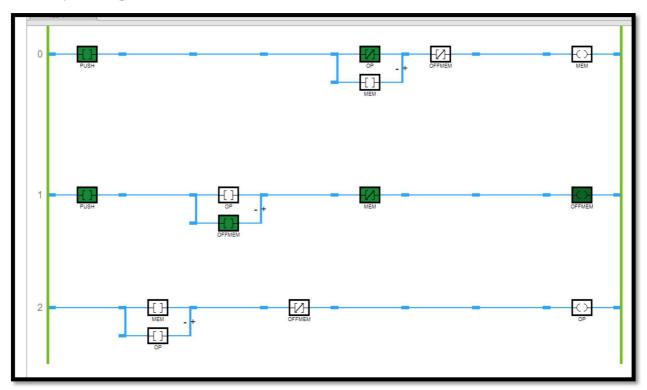

b) Two lights are ON.

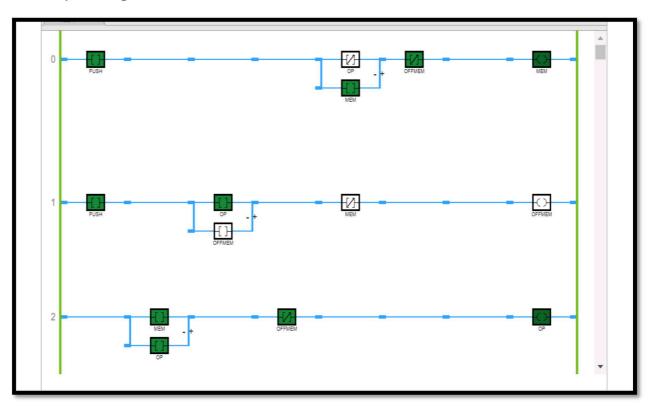

			Name:					
	Pallaui Gaik	mi, aaikwad						
	142103005							
0.4	Sensons and Automation. Assignment No: 6							
91.	PLC block	diagram, appl	ha mitain					
	vendores	of PLC.	w=					
\rightarrow		0						
		Pour						
		Power						
		114 0						
		Processor						
0		I						
marte	- Jidan	Programming	output					
Sensor		device		-				
•	Applications:							
1.	Triaffic Industry Signal							
2.	Triaffic Industry Signal Sutomotive Industry							
3	Paper Industry							
4,	ofteel Indiestry							
5.	Chemical Industry. Crease Industry							
6.	Crlass ?	Industry						
•	Vendore:							
1.	Siemens							
2.	Omyon							
3 '	Scheider							
5 me - 1								

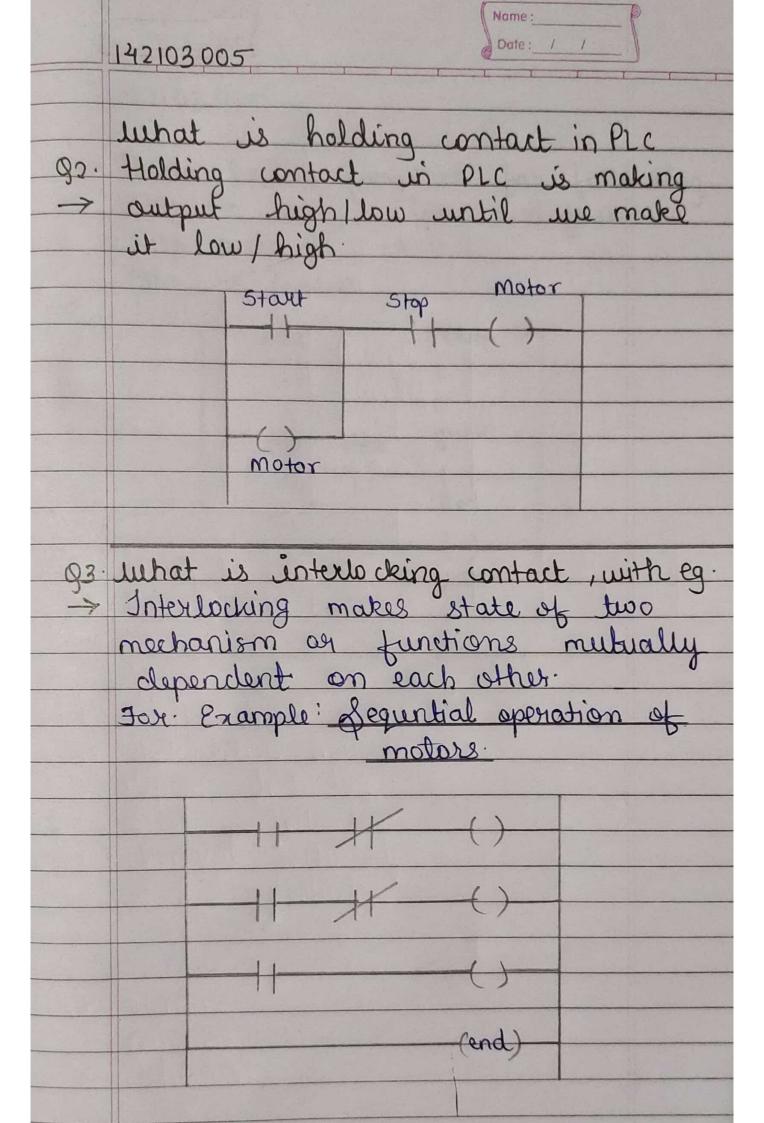

14	2103000		5	Nome: Date: / /
	Haw lo $B1 \rightarrow B1$ $B2 \rightarrow$		gram blue > Red	for following and green
		PB1	Blue	
		PB1 PB2	green () Red	
		11	green	